

3rd July 2013 The simplest FM Crystal Radio

The simplest battery-free FM Crystal Radio.

Make the world's simplest battery-free FM crystal radio

Only consists of two high frequency diode: 1N34A or ISS86 or ISS106.

A 100K Resistor.


An 1.8M antenna.

And a crystal or high impedance earphone




[http://1.bp.blogspot.com/-x9lr6oLJ9z8/UdQ_IBNismI/AAAAAAAAABQE/pfbpj7x0Azs/s1600/IMG_2607.JPG]

Refer to this circuit diagram

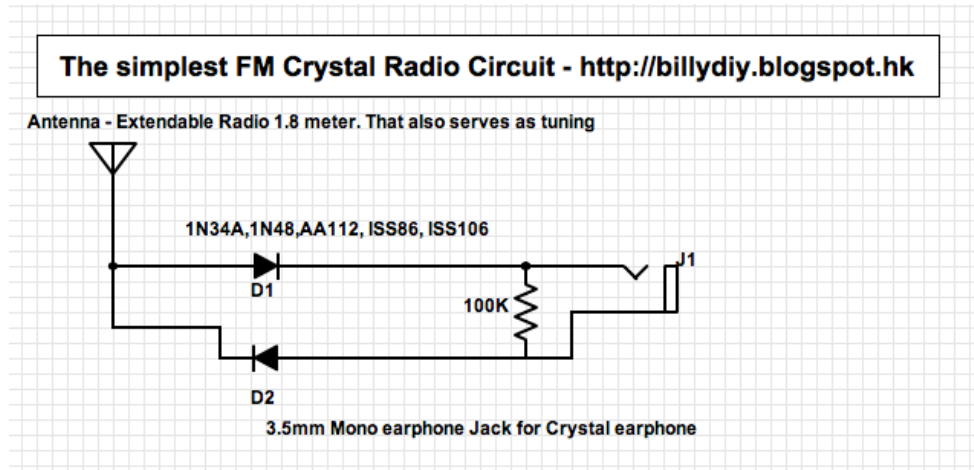

[<http://2.bp.blogspot.com/->

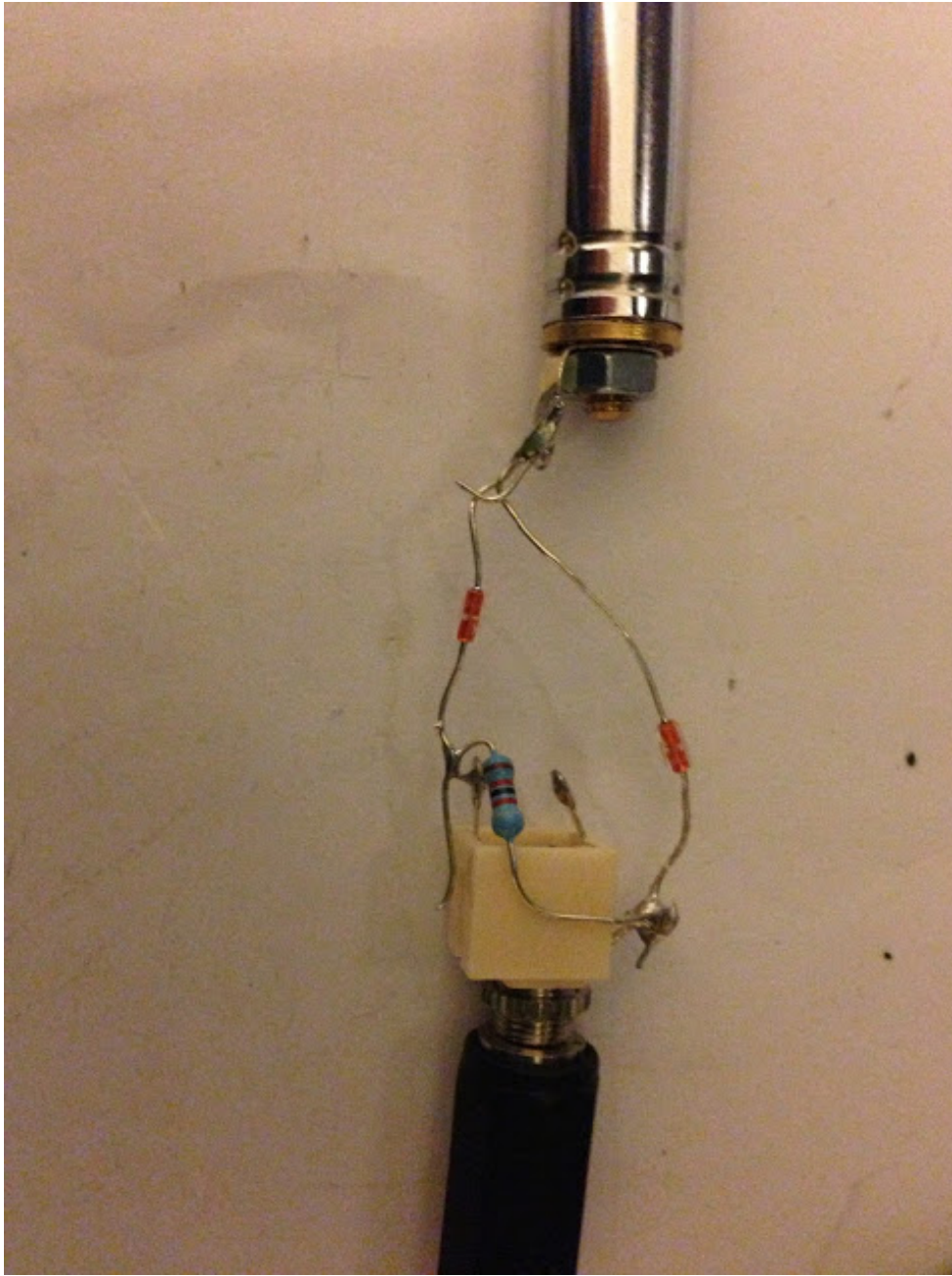[G9onfk5x8FA/UdRDYhFFyAI/AAAAAAAAABRA/mtiP8wFX78E/s639/Screen+Shot+2013-07-03+at+11.28.54+PM.png](http://2.bp.blogspot.com/-G9onfk5x8FA/UdRDYhFFyAI/AAAAAAAAABRA/mtiP8wFX78E/s639/Screen+Shot+2013-07-03+at+11.28.54+PM.png)]



[http://4.bp.blogspot.com/-UVDtJdx6leQ/UdQ_IE_swzI/AAAAAAAAABQM/ToNTHsm8pdc/s1600/IMG_2608.JPG]
]



[http://1.bp.blogspot.com/-jvFTM9CBpKQ/UdQ_kx4Q35I/AAAAAAAAABQA/W1wxPV0ezZk/s1600/IMG_2609.JPG]

Posted 3rd July 2013 by [Billy](#)

Start Download

Search Videos W/ HowToSimplified On How To Do It Yourself - Free! Go to howtosimplified.com



0 Add a comment

Enter your comment...

Comment as: Unknown (Goo ▼)

Sign out

Publish

Preview

☐ Notify me